


	<u>NAND</u>	<u>NOR</u>
NOT	1	1
AND	2	3
OR	3	2

Implementation of all logic gates using NAND gate


NOT gate:



AND gate:

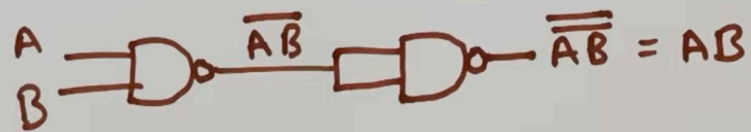

OR gate:

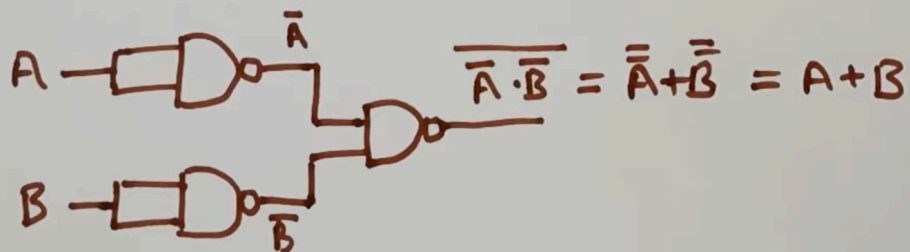

Implementation of logic gates using NOR gate

NOT gate:



OR gate:



AND gate:

